

Custom Search

Geeks Classes


Login

Write an Article

## Digital logic | Carry Look-Ahead Adder
 
### Motivation behind Carry Look-Ahead Adder :

In ripple carry adders, for each adder block, the two bits that are to be added are available instantly. However, each adder block waits for the carry to arrive from its previous block. So, it is not possible to generate the sum and carry of any block until the input carry is known. The  $i^{th}$  block waits for the  $i - 1^{th}$  block to produce its carry. So there will be a considerable time delay which is carry propagation delay.




Consider the above 4-bit ripple carry adder. The sum  $S_4$  is produced by the corresponding full adder as soon as the input signals are applied to it. But the carry input  $C_4$  is not available on its final steady state value until carry  $C_3$  is available at its steady state value. Similarly  $C_3$  depends on  $C_2$  and  $C_2$  on  $C_1$ . Therefore, though the carry must propagate to all the stages in order that output  $S_3$  and carry  $C_4$  settle their final steady-state value.

The propagation time is equal to the propagation delay of each adder block, multiplied by the number of adder blocks in the circuit. For example, if each full adder stage has a propagation delay of 20 nanoseconds, then  $S_3$  will reach its final correct value after 60 ( $20 \times 3$ ) nanoseconds. The situation gets worse, if we extend the number of stages for adding more number of bits.
 
### Carry Look-ahead Adder :

A carry look-ahead adder reduces the propagation delay by introducing more complex hardware. In this design, the ripple carry design is suitably transformed such that the carry logic over fixed groups of bits of the adder is reduced to two-level logic. Let us discuss the design in detail.



A	B	C	C +1	Condition
0	0	0	0	No Carry Generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No Carry Propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry Generate
1	1	1	1	

Consider the full adder circuit shown above with corresponding truth table. We define two variables as 'carry generate'  $G_i$  and 'carry propagate'  $P_i$  then,

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The sum output and carry output can be expressed in terms of carry generate  $G_i$  and carry propagate  $P_i$  as



$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

where  $G_i$  produces the carry when both  $A_i, B_i$  are 1 regardless of the input carry.  $P_i$  is associated with the propagation of carry from  $C_i$  to  $C_{i+1}$ .

The carry output Boolean function of each stage in a 4 stage carry look-ahead adder can be expressed as

$$C_1 = G_0 + P_0 C_{in}$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 P_0 C_{in}$$

From the above Boolean equations we can observe that  $C_4$  does not have to wait for  $C_3$  and  $C_2$  to propagate but actually  $C_4$  is propagated at the same time as  $C_3$  and  $C_2$ . Since the Boolean expression for each carry output is the sum of products so these can be implemented with one level of AND gates followed by an OR gate.

 The implementation of three Boolean functions for each carry output ( $C_2, C_3$  and  $C_4$ ) for a carry look-ahead carry generator shown in below figure.



#### Time Complexity Analysis :

We could think of a carry look-ahead adder as made up of two “parts”



1. The part that computes the carry for each bit.
2. The part that adds the input bits and the carry for each bit position.

The  $\log(n)$  complexity arises from the part that generates the carry, not the circuit that adds the bits.

Now, for the generation of the  $n^{th}$  carry bit, we need to perform a AND between  $(n+1)$  inputs. The complexity of the adder comes down to how we perform this AND operation. If we have AND gates, each with a fan-in (number of inputs accepted) of  $k$ , then we can find the AND of all the bits in  $\log_k(n + 1)$  time. This is represented in asymptotic notation as  $\Theta(\log n)$ .

### Advantages and Disadvantages of Carry Look-Ahead Adder :

#### Advantages –

- The propagation delay is reduced.
- It provides the fastest addition logic.

#### Disadvantages –

- The Carry Look-ahead adder circuit gets complicated as the number of variables increase.
- The circuit is costlier as it involves more number of hardware.

### GATE CS Corner Questions

Practicing the following questions will help you test your knowledge. All questions have been asked in GATE in previous years or in GATE Mock Tests. It is highly recommended that you practice them.

1. [GATE CS 2016 \(Set-1\), Question 43](#)
2. [GATE CS 2004, Question 90](#)
3. [GATE CS 2007, Question 85](#)
4. [GATE CS 2006, Question 85](#)
5. [GATE CS 1997, Question 15](#)

#### References –

[iitkgp.virtual-labs](http://iitkgp.virtual-labs)

[Carry-lookahead adder – Wikipedia](#)



**Samujjal Das**

Check out this Author's [contributed articles](#).



If you like GeeksforGeeks and would like to contribute, you can also write an article using [contribute.geeksforgeeks.org](https://contribute.geeksforgeeks.org) or mail your article to [contribute@geeksforgeeks.org](mailto:contribute@geeksforgeeks.org). See your article appearing on the GeeksforGeeks main page and help other Geeks.

Please write comments if you find anything incorrect, or you want to share more information about the topic discussed above.

Digital Electronics & Logic Design GATE CS

[Login to Improve this Article](#)

Please write to us at [contribute@geeksforgeeks.org](mailto:contribute@geeksforgeeks.org) to report any issue with the above content.

## Recommended Posts:

[Mathematics | Graph theory practice questions](#)

[Operating System | Process Table and Process Control Block \(PCB\)](#)

[Data Communication | Transmission Impairment](#)

[Digital logic | Master Slave JK Flip Flop](#)

[Digital Logic | Parallel Adder & Parallel Subtractor](#)

[Digital Logic | Implicants in K-Map](#)

[Non-Restoring Division For Unsigned Integer](#)

[Restoring Division Algorithm For Unsigned Integer](#)

[Amortized analysis for increment in counter](#)

[Digital Electronics | Operational Amplifier \(op-amp\)](#)

(Login to Rate)

0

Average Difficulty : **0/5.0**  
No votes yet.

☐  
☐

Add to TODO List

Mark as DONE

Basic

Easy

Medium

Hard

Expert

Writing code in comment? Please use [ide.geeksforgeeks.org](https://ide.geeksforgeeks.org), generate link and share the link here.

Load Comments

Share this post!



## A computer science portal for geeks

710-B, Advant Navis Business Park,  
Sector-142, Noida, Uttar Pradesh - 201305  
[feedback@geeksforgeeks.org](mailto:feedback@geeksforgeeks.org)

### COMPANY

About Us  
Careers  
Privacy Policy  
Contact Us

### PRACTICE

Company-wise  
Topic-wise  
Contests  
Subjective Questions

### LEARN

Algorithms  
Data Structures  
Languages  
CS Subjects  
Video Tutorials

### CONTRIBUTE

Write an Article  
GBlog  
Videos

@geeksforgeeks, Some rights reserved

